

SELF ASSESSMENT TEST SOLUTIONS

1. $R \propto l, \dots\dots (1)$

$R \propto \frac{1}{A} \dots\dots (2)$

$R \propto \frac{l}{A}$

$\Rightarrow R = \rho \frac{l}{A}$ where ρ is the electrical resistivity.

S.I. unit of resistivity, $\rho = \frac{RA}{l} = \frac{\text{ohm} \times \text{m}^2}{\text{m}} = \text{ohm} \times \text{m}$

(b) $\rho = \frac{RA}{l} = \frac{100 \times 3 \times 10^{-7}}{5} = 60 \times 10^{-7} \text{ ohm} \times \text{m}$

2. (i) Resistance of a uniform metallic conductor is directly proportional to its length (l) and inversely proportional to the area of cross-section (A).

i.e., $R \propto l \rightarrow (1)$

and $R \propto \frac{1}{A} \rightarrow (2)$

Combining equations (1) and (2),


$R \propto \frac{l}{A}$

i.e., $R = \rho \frac{l}{A}$, where ρ is a constant of proportionality

and is called electrical resistivity.

(b) $R = \rho \frac{l}{A} = 2.8 \times 10^{-8} \times \frac{4}{1.50 \times 10^{-6}} = 7.46 \times 10^{-2} \Omega$


3.

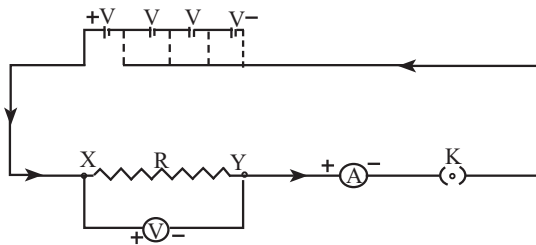


The value of I increases as V increases.

i.e., $V \propto I$ or $V = IR$

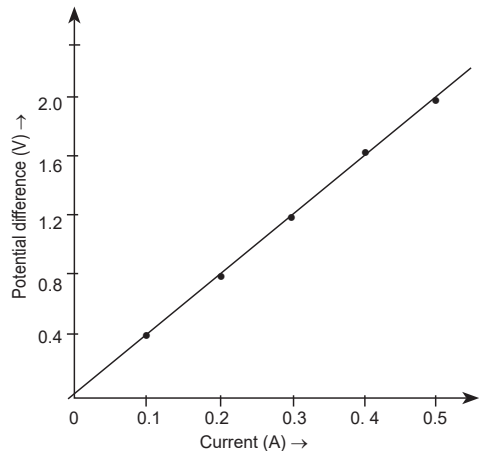$R = \frac{V}{I} = \frac{1}{0.25} = 4\Omega$



4. (i)

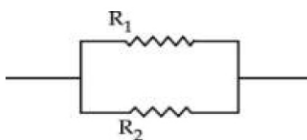

(ii) Given, $R_1 = 4\Omega$, $R_2 = 8\Omega$,

SELF ASSESSMENT TEST SOLUTIONS

Since the resistors are connected in parallel, V remains same.

$$\therefore I_1 = \frac{V}{R_1} = \frac{V}{4} \text{ and } I_2 = \frac{V}{R_2} = \frac{V}{8}$$

$$\therefore I_1 : I_2 = \frac{V/4}{V/8} = \frac{8}{4} = 2 : 1$$

5. (i) When coil A or B is used separately

$$I = \frac{V}{R_A} = \frac{V}{R_B} = \frac{220}{30} = 7.33 \text{ A}$$

- (ii) When the two coils are arranged in series, the total resistance,

$$R_s = R_A + R_B = 30 + 30 = 60\Omega$$

$$\therefore I = \frac{V}{R_s} = \frac{220V}{60\Omega} = 3.67 \text{ A}$$

- (iii) When the two coils are arranged in parallel the total resistance,

$$\frac{1}{R_p} = \frac{1}{R_A} + \frac{1}{R_B} = \frac{1}{30} + \frac{1}{30} = \frac{2}{30} = \frac{1}{15}$$

$$\Rightarrow R_p = 15\Omega$$

$$\therefore I = \frac{V}{R_p} = \frac{220}{15} = 14.67 \text{ A}$$

6. (a) In series arrangement, same current will flow through all the appliances which is not required and the equivalent resistance becomes higher hence the current drawn becomes less.


(b) Given, $V = 2.5 \text{ V}$, $I = 500\text{mA} = 0.5\text{A}$

(i) Power = $VI = 2.5 \times 0.5 = 1.25 \text{ W}$

(ii) Resistance, $R = \frac{V}{I} = \frac{2.5}{0.5} = 5\Omega$

(iii) Energy consumed = $P \times t = 1.25 \times 4 = 5\text{wh}$

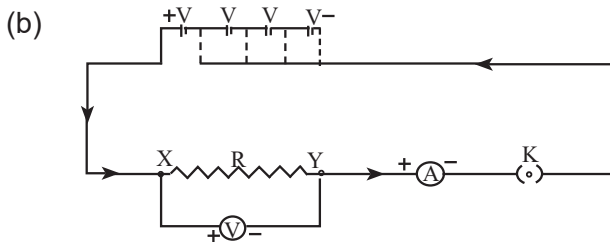7. (a) Ohm's law : According to this law, the electric current flowing through a metallic conductor is directly proportional to the potential difference across its ends, provided its temperature remains the same.



- (c) Since R_1 and R_2 are connected in parallel, their effective resistance,

SELF ASSESSMENT TEST SOLUTIONS

$$\frac{1}{R_p} = \frac{1}{2} + \frac{1}{1} = \frac{3}{2}$$


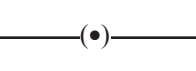
$$\Rightarrow R_p = \frac{2}{3} \Omega = 0.66 \Omega$$

Now R_3 is in series with R_p .

$$\therefore \text{Effective resistance} = R_3 + R_p = 3\Omega + 0.66\Omega = 3.66 \Omega$$

8. Voltmeter is used to measure the P.D between two points. One volt is the potential difference between two points in a current carrying conductor when 1 joule of work is done to move a charge of 1 coulomb from one point to the other.

$$1 \text{ volt} = \frac{1 \text{ Joule}}{1 \text{ Coulomb}}$$

(i) Variable resistor:  (ii) Plug key which is closed: 

(i) Circuit I (ii) Circuit II (iii) Circuit II (iv) Circuit I

9. • kW is the unit of power whereas kWh is the unit of energy.

$$\bullet \quad (i) \quad I = \frac{P}{V} = \frac{4.4\text{kW}}{220\text{V}} = \frac{4400}{220} = 20 \text{ A}$$

$$(ii) \quad R = \frac{V^2}{P} = \frac{220 \times 220}{4400} = 11 \Omega$$

$$(iii) \quad E = P \times t = 4.4 \text{ kW} \times 5 \text{ h} = 22 \text{ kWh}$$

$$(iv) \quad \text{Cost} = 22 \times 6.5 = \text{Rs.}143$$

10. (i) When 1 ampere current flows through a conductor whose potential difference is 1 volt, then resistance is 1ohm.

$$(ii) \quad R_s = R_1 + R_2 = 24 \Omega$$

$$\frac{1}{R_p} = \frac{1}{12} + \frac{1}{12} = \frac{2}{12} = \frac{1}{6}$$

$$\Rightarrow R_p = 6\Omega$$

$$\text{Power consumed in series combination, } P_s = \frac{V^2}{R_s} = \frac{6 \times 6}{24} = 1.5\text{W}$$

$$\text{Power consumed in parallel combination, } P_p = \frac{V^2}{R_p} = \frac{6 \times 6}{6} = 6\text{W}$$

$$\text{Ratio} = \frac{P_s}{P_p} = \frac{1.5}{6} = \frac{1}{4} = 1 : 4$$

- (iii) Voltmeter is connected in parallel across the two points in the circuit.